



Project Report: Traffic Light Controller

Team 3 Members: Andrew Mousad, Libin Jian, Jerome Poonvichit, Mohamed Khalifa


Introduction:

For this project, a Finite State Machine (FSM), specifically a Moore Machine is being utilized and implemented into a traffic light controller system. The outputs will turn the LEDs on the FPGA board on and off based on the use of timers, FSM and a clock divider. For the timer, a clock divider is required to reduce the speed of the board's clock in order to be able to time each state. As for the LEDs, the LEDs on top of the switches on the FPGA board are used for this project.

System Diagram / State Diagram:

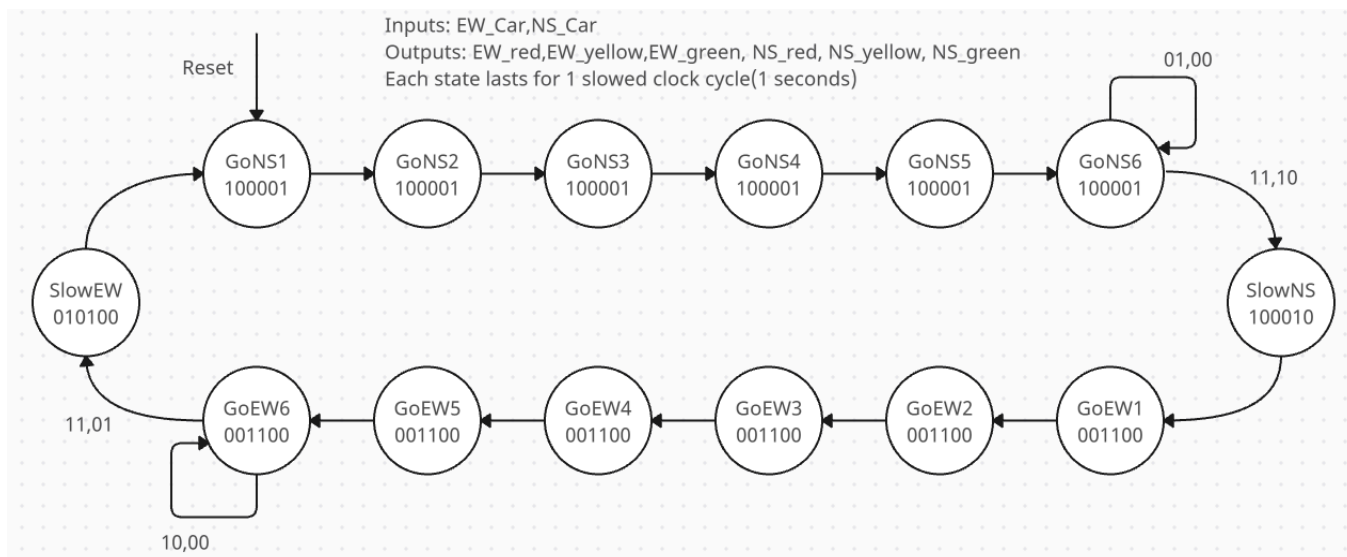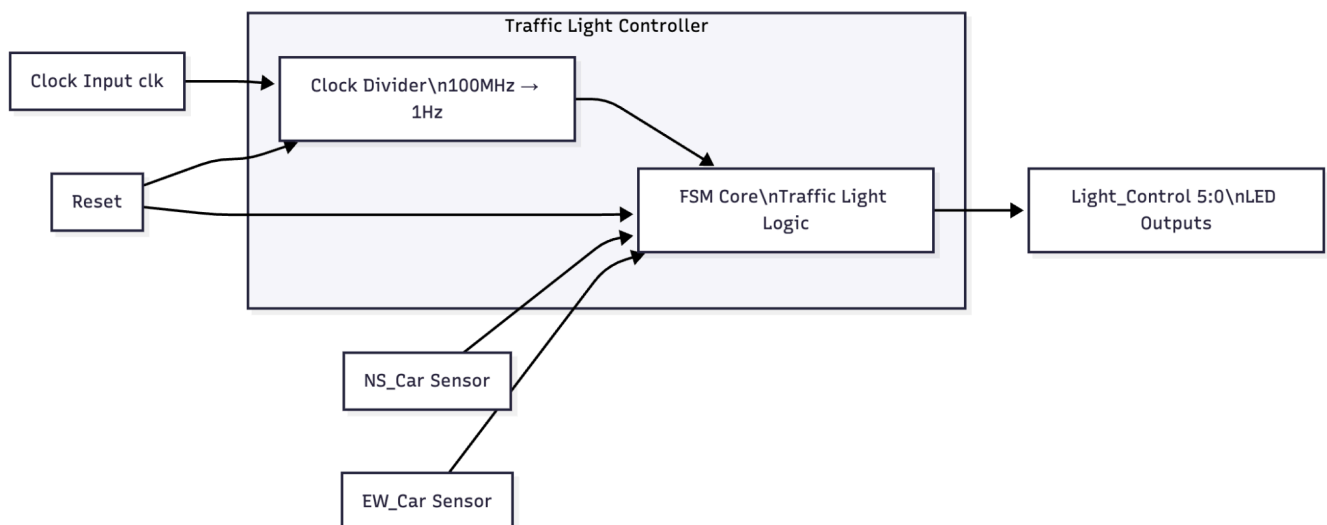

RTL Schematic:

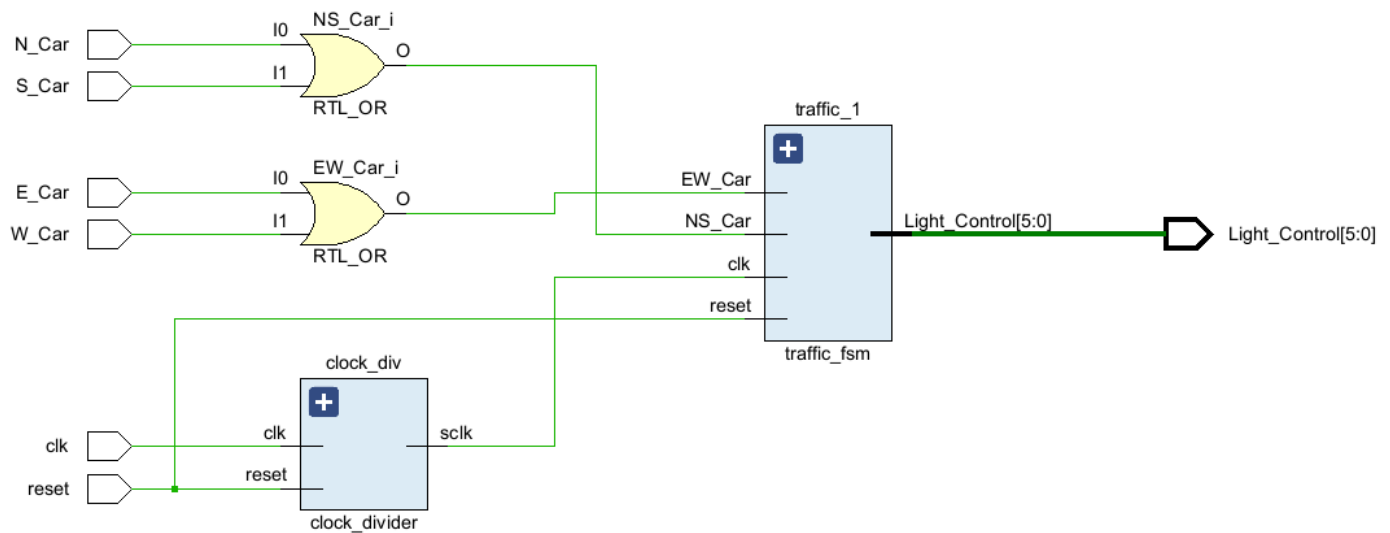

Post-Implementation Area / Power / Static Timing Report:


Name	Slice LUTs (32600)	Slice Registers (65200)	Slice (8150)	LUT as Logic (32600)	Bonded IOB (210)	BUFGCTRL (32)
traffic_light_controller	47	43	23	47	10	1

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.696 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 28.3°C
Thermal Margin: 71.7°C (14.9 W)
Ambient Temperature: 25.0 °C
Effective θJA: 4.8°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

Total On-Chip Power: 0.696 W

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 5.875 ns	Worst Hold Slack (WHS): 0.202 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 33	Total Number of Endpoints: 33	Total Number of Endpoints: 34

All user specified timing constraints are met.

Demonstration:

[demo.mp4](#)

Discussion:

For this project, we built a working traffic light controller using a Moore Machine. The clock divider enables real-time LED timing to slow down the FPGA clock. We also implemented state changes based on N, S, E, and W emulating sensors of the car's direction as button inputs. Moreover, we verified the correct transitions and light outputs on the FPGA board. Lastly, we demonstrated key ECE 446 concepts such as FSM design, timing, and sequential logic.

Challenges:

The challenges we faced were mainly deciding how many states we want to include for a smooth traffic flow and to be able to distinguish between each result. This included making sure the LED light patterns clearly matched each traffic phase. In addition, we also needed to adjust the clock speed so the demonstration will look clean and easy to follow. We also needed to ensure the sensors, Northsouth (NS) and Eastwest (EW) buttons, triggered the state changes at the right moment.

If we were to redo this project, we would implement the RGB LEDs on the FPGA board to show the color of the traffic lights. This would make the traffic light easier to understand, rather than having to look at the positions of the lit LEDs.

References:

<https://www.chipverify.com/verilog/verilog-fsm#verilog-fsm-structure>

Appendix

Verilog Code:

traffic_light_controller.v:

```
`timescale 1ns / 1ps

module traffic_light_controller(
    input N_Car,
    input S_Car,
    input E_Car,
    input W_Car,
    input clk,
    input reset,
    output [5:0] Light_Control
);
    wire NS_Car, EW_Car;
    wire slow_clk;
    assign NS_Car = N_Car | S_Car;
    assign EW_Car = E_Car | W_Car;

    // clock divider divides the system clock into a 1-second clock
    clock_divider clock_div1(
        .sclk(slow_clk),
        .clk(clk),
        .reset(reset)
    );
    traffic_fsm traffic_1(
        .NS_Car(NS_Car),
        .EW_Car(EW_Car),
        .clk(slow_clk),
        .reset(reset),
        .Light_Control(Light_Control)
    );
endmodule
```

Traffic_fsm.v:

```
`timescale 1ns / 1ps

module traffic_fsm(
    input NS_Car,
    input EW_Car,
    input clk,
    input reset,
    output reg [5:0] Light_Control
);
    wire NS_Car, EW_Car, clk, reset;
    reg [3:0] current_state, next_state;
    // each state will last for 1 clock cycle and with clock divider, a clock cycle is 1 second
```

```

parameter GoNS1 = 4'b0001, GoNS2 = 4'b0010, GoNS3 = 4'b0011, GoNS4 = 4'b0100, GoNS5 =
4'b0101, GoNS6 = 4'b0110, // NS green, EW red
    SlowNS = 4'b0111, // NS yellow, EW red
    GoEW1 = 4'b1000, GoEW2 = 4'b1001, GoEW3 = 4'b1010, GoEW4 = 4'b1011, GoEW5 = 4'b1100,
GoEW6 = 4'b1101, // EW green, NS red
    SlowEW = 4'b1110; // EW yellow, NS red

// light bits follow: EWred, EWyellow, EWgreen, NSred, NSyellow, NSgreen
parameter [5:0] GoNS_light = 6'b100001, SlowNS_light = 6'b100010,
    GoEW_light = 6'b001100, SlowEW_light = 6'b010100;

// update current state on posedge clock with asynchronous reset
always @(posedge(clk), posedge(reset))
begin
    if(reset)
        current_state <= GoNS1;
    else
        current_state <= next_state;
end

// next state logic
always@(*)
begin
    case(current_state)
        GoNS1, GoNS2, GoNS3, GoNS4, GoNS5, GoEW1, GoEW2, GoEW3, GoEW4, GoEW5: // lights will
finish their cycle regardless of input
        next_state = current_state + 1;
        GoNS6: // NS lights will change if there are cars detected on EW
        if(NS_Car & ~EW_Car)
            next_state = GoNS6;
        else if(NS_Car & EW_Car)
            next_state = SlowNS;
        else if(EW_Car & ~NS_Car)
            next_state = SlowNS;
        else if(~NS_Car & ~EW_Car)
            next_state = GoNS6;
        GoEW6: // EW lights will change if there are cars detected on NS
        if(~NS_Car & EW_Car)
            next_state = GoEW6;
        else if(EW_Car & NS_Car)
            next_state = SlowEW;
        else if(~EW_Car & NS_Car)
            next_state = SlowEW;
        else if(~EW_Car & ~NS_Car)
            next_state = GoEW6;
        SlowNS: // next state will be GoEW1
        next_state = GoEW1;
        SlowEW: // next state will be GoNS1
        next_state = GoNS1;
    endcase
end

```

```

    default:
        next_state = GoNS1;
    endcase
end
// LED output is clocked
always @(posedge(clk))
begin
    case(current_state)
        GoNS1, GoNS2, GoNS3, GoNS4, GoNS5, GoNS6: begin
            Light_Control <= GoNS_light;
        end
        GoEW1, GoEW2, GoEW3, GoEW4, GoEW5, GoEW6: begin
            Light_Control <= GoEW_light;
        end
        SlowNS: begin
            Light_Control <= SlowNS_light;
        end
        SlowEW: begin
            Light_Control <= SlowEW_light;
        end
        default: begin
            Light_Control <= Light_Control;
        end
    endcase
end
endmodule

```

clock_divider.v:

```

module clock_divider(

input clk,
input reset,
output reg sclk
);
reg [31:0] count;
always@(posedge clk or posedge reset)
begin
    if(reset == 1'b1) begin
        count <= 32'd0;
        sclk <= 1'b0;
    end else begin
        if(count == 32'd50000000) begin //50000000 for 1 sec 250000000 for 5 sec
            count <= 32'd0;
            sclk <= ~sclk;
        end else begin
            count <= count + 1;
        end
    end
end
end

```

endmodule